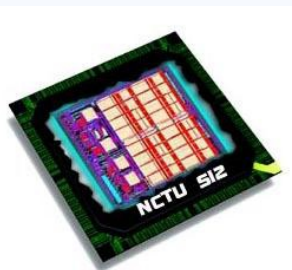


# SEQUENTIAL CIRCUITS I

**NCTU-EE IC LAB SPRING-2023**



Lecturer: YU-HUA LUO



# Outline

- ✓ **Section 1 Sequential Circuits**
- ✓ **Section 2 Finite State Machine**
- ✓ **Section 3 Timing**
- ✓ **Section 4 Synthesis and Design Compiler**



# Outline

## ✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ Reset


✓ Coding Style

✓ Generate & For loop



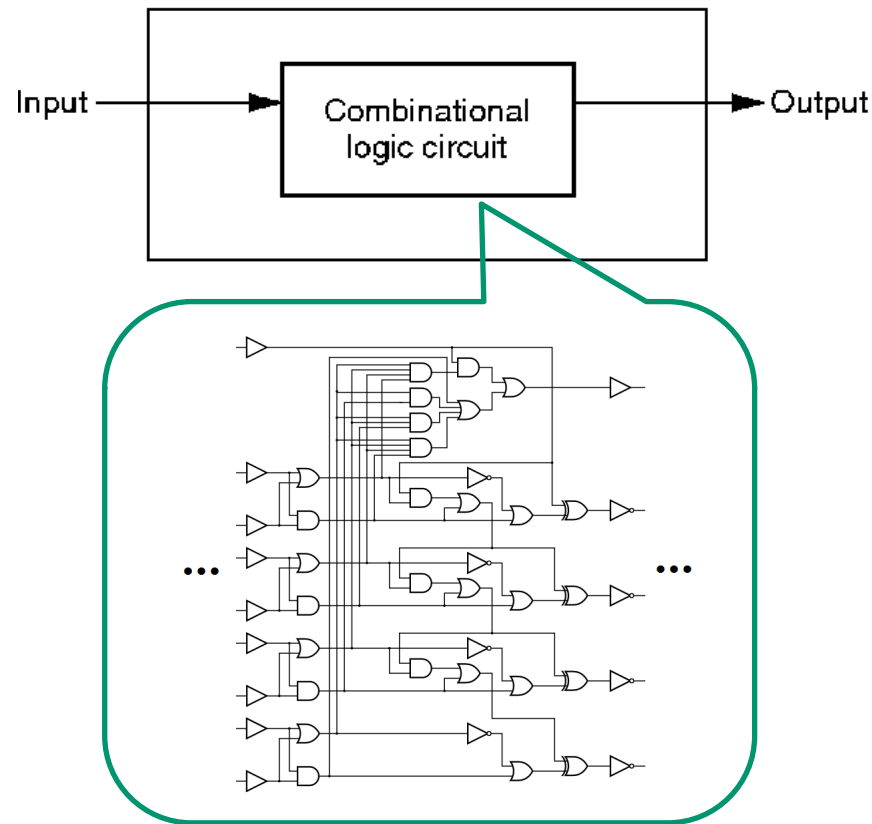
# Motivation

- ✓ **Progress so far : Combinational circuit**
  - Output is only a function of the **current** input values


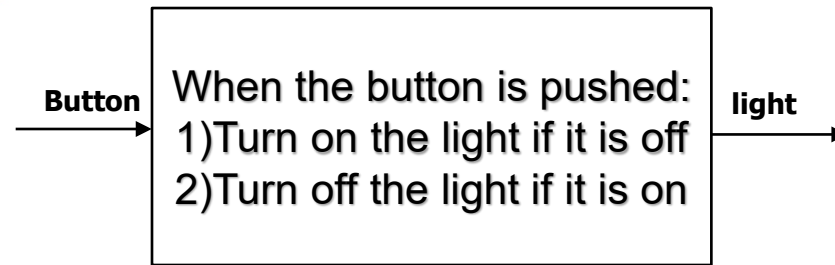
# Motivation

- ✓ What if you were given the following design specification:



- ✓ What makes this circuit so different from we've discussed before?

**“State”**




# What is Sequential Circuit ?

## ✓ Sequential circuit

- Output depends not only on the current input values, but also on **preceding** input values
- It remembers sort of the past history of the system


## ✓ How?

- Registers(Flip-Flops)

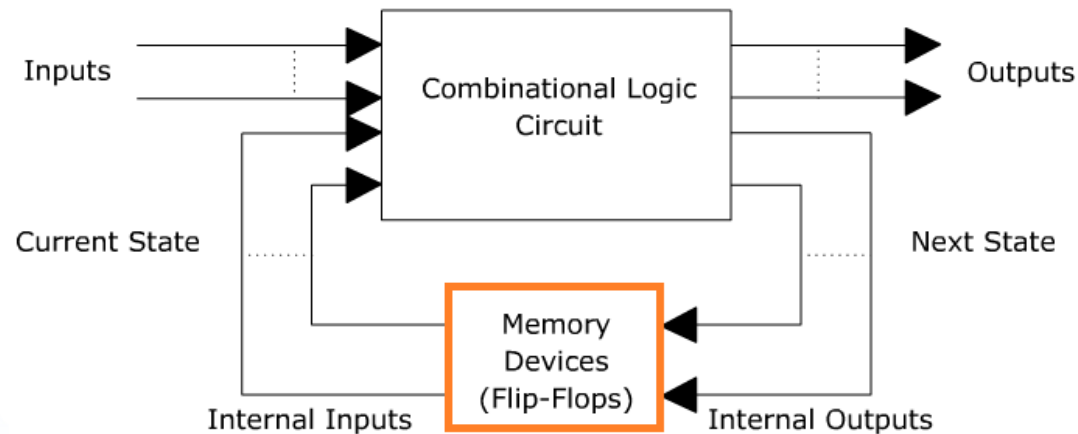

# Latch Operation


## ✓ Latch: level sensitive

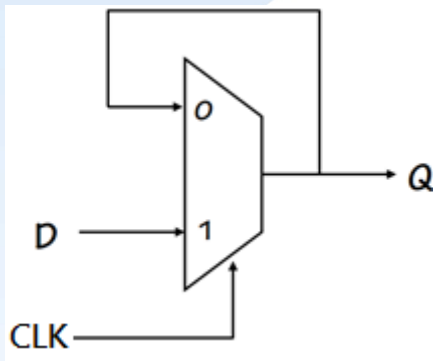

CLK	D	Q	Q'	
0	--	0	0	} Q stable
0	--	1	1	
1	0	--	0	} Q follows D
1	1	--	1	

CLK=1 : Q follows D

CLK=0 : Q holds


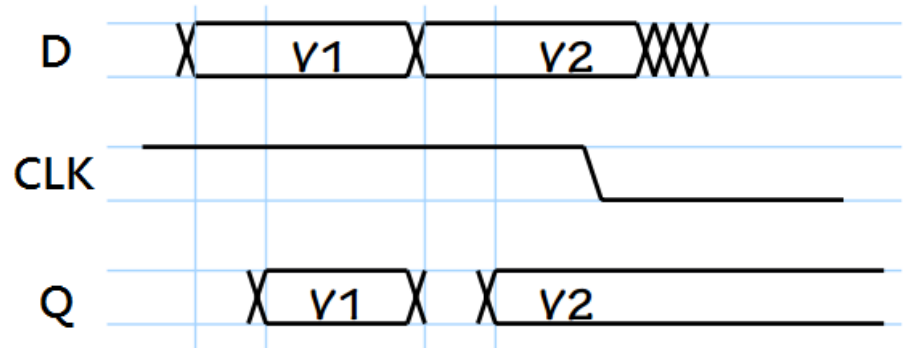


# Avoid Unintentional Latch (1/2)
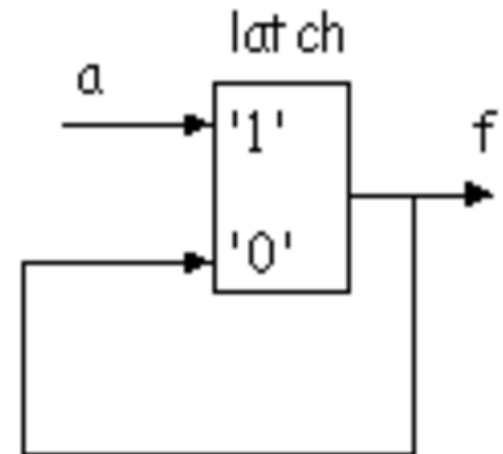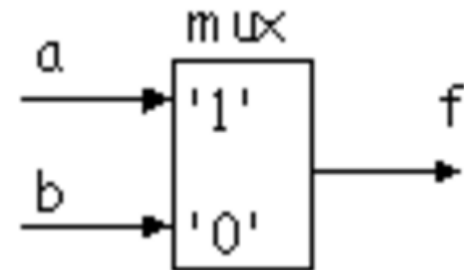
## ✓ Example

```
always @(*)
begin
    if(sel == 1) f = a;
    else f = b;
end
```

```
always @(*)
begin
    if(sel == 1) f = a;
end
```





# Avoid Unintentional Latch (2/2)

## ✓ Avoid latches in combinational circuit

- Avoid incomplete if-then-else
- Avoid incomplete case statements

X

```
if(!rst_n) out = 0;  
else if(m==3'd0) out = m0_out;  
else if(m==3'd1) out = m1_out;
```

X

```
case(mode)  
  3'd0: out = m0_out;  
  3'd1: out = m1_out;  
endcase
```

O

```
if(!rst_n) out = 0;  
else if(m==3'd0) out = m0_out;  
else if(m==3'd1) out = m1_out;  
else out = default_out;
```

O


```
case(mode)  
  3'd0: out = m0_out;  
  3'd1: out = m1_out;  
default:  
  out = default_out;  
endcase
```



# Avoid Combinational Feedback (1/2)

## ✓ Example

```
assign out=out+1;
```

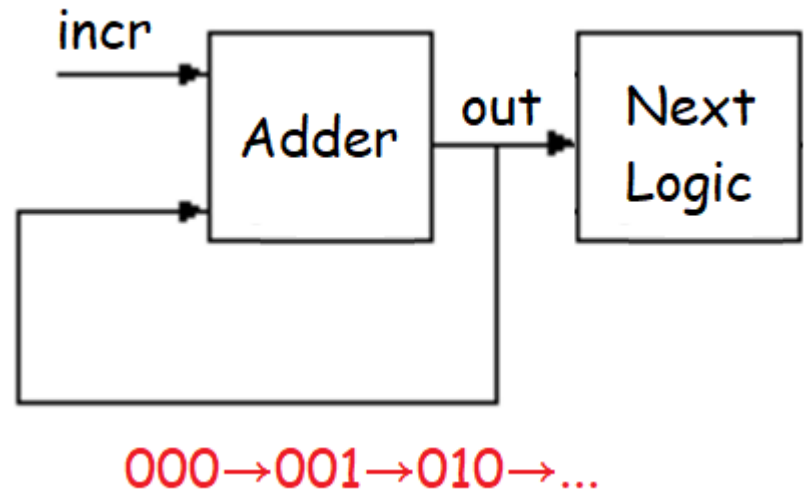

# Avoid Combinational Feedback (2/2)

## ✓ Avoid combinational feedbacks

- Lead to unpredictable oscillated output
- NOT allowed

X

```
assign a=a+1;
```

X

```
always @(*) begin  
    a = a+1;  
end
```

X

```
always @(*) begin  
    if(in_a) a = c;  
    else a = a;  
end
```

X

```
assign out_value=out;  
always @(*) begin  
    case(mode)  
        3'd0: out = m0_out;  
        3'd1: out = m1_out;  
        default:  
            out = out_value;  
    endcase  
end
```




# Avoid Latch Summary

- ✓ **In a sequential circuit -- with clk control**
  - It is a flip-flop so there is not a latch problem.
- ✓ **In a combinational circuit -- without clk control**
  - If some net needs to keep its data, DC will synthesize a latch.
- ✓ **How to avoid?**
  - Conditional statement : must be full cases
  - Otherwise it will produce latches.
    - if – else work together or add default value
  - Ex: if ( a== b) c = 1 ;
  - Case statement : remember default value
  - Ex: case (a) 1'b0: c = b; endcase
  - Avoid combinational feedback
- ✓ **Notice**
  - In a combinational circuit, no information will be stored, so latches are not allowed.
- ✓ **Latch is a memory storage device**
  - It will cause the problems of timing analysis .
    - That's why we recommend to avoid latches here!!




# Flip-Flop Operation

✓ D flip-flop: edge triggered

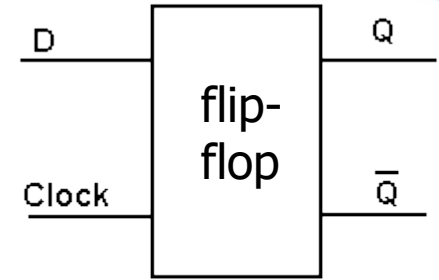


✓ Positive latch v.s. positive D flip-flop

Latch ( level triggered )

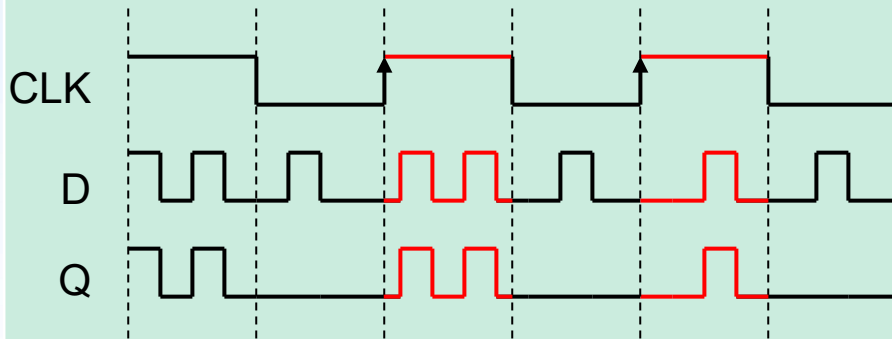


D flip-flop ( edge triggered )

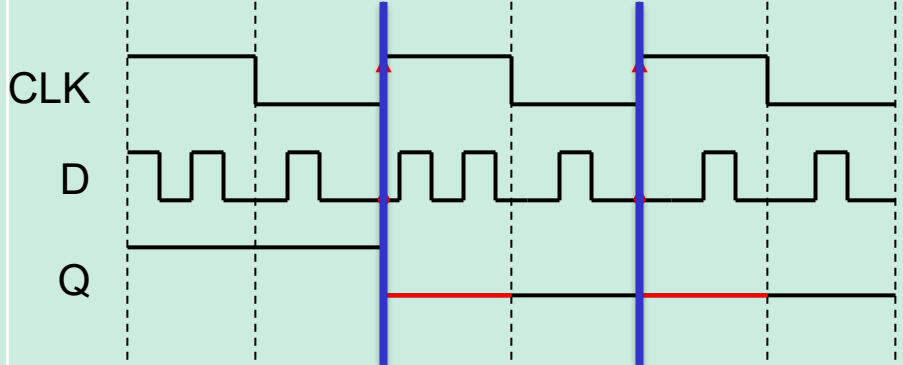

# Flip-Flop Data Type
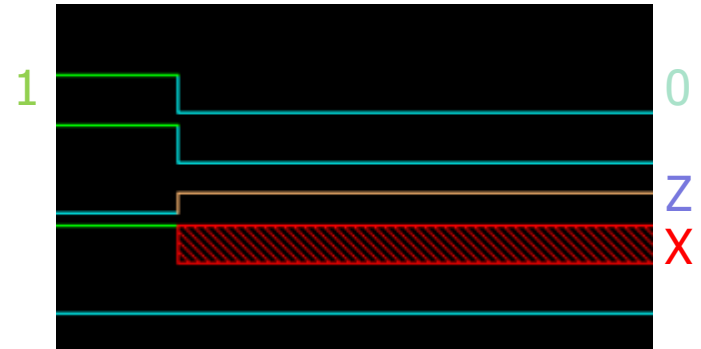
## ✓ Flip-flop: data storage element with 4 states (0,1, X, Z)

- **0**: logic low
- **1**: logic high
- **X**: unknown, may be a 0,1, Z, or in transition
- **Z**: high impedance, floating state



## ✓ Operations on the 4 states

- Example: AND, OR, NOT gate


AND	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

OR	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

NOT	output
0	1
1	0
X	X
Z	X
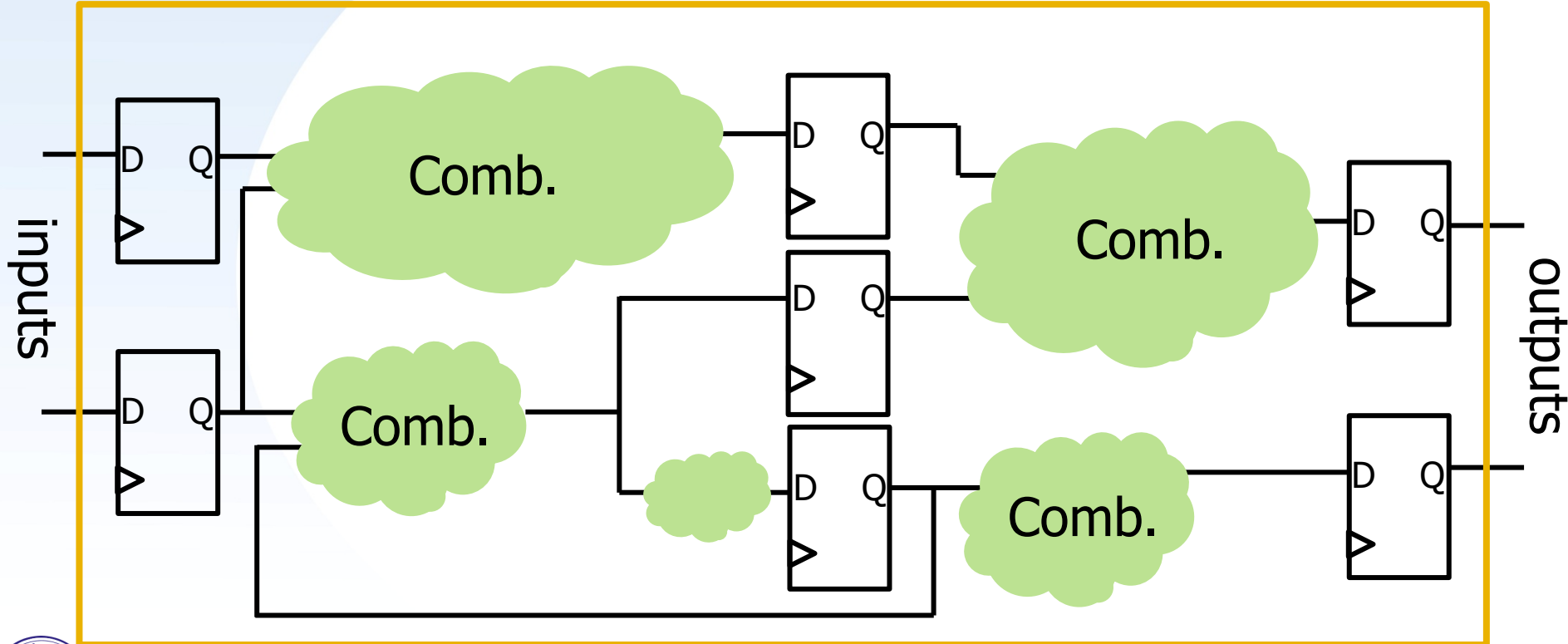
# Concept of Sequential Circuit

- ✓ Most computations are done by combinational circuit
  - ✓ Sequential elements are used for storage
- top design



# Outline

## ✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ Reset

✓ Coding Style

✓ Generate & For loop





# Blocking & Non-blocking

## ✓ Blocking assignment & Non-blocking assignment

### Blocking


```
always @(a or b or c)
begin
    x = a & b;
    y = x | c;
end
```

Blocking behavior	a	b	c	x	y
initial condition	1	1	0	1	1
a changes 1 -> 0	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x   c;	0	1	0	0	0

### Non-blocking

```
always @(a or b or c)
begin
    x <= a & b;
    y <= x | c;
end
```

non-blocking behavior	a	b	c	x	y
initial condition	1	1	0	1	1
a changes 1 -> 0	0	1	0	1	1
x <= a & b; y <= x   c;	0	1	0	0	1

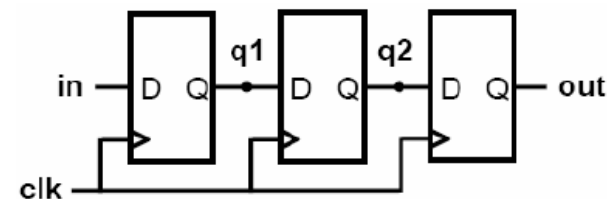

### Shift register behavior




# Assignment in Sequential Circuit

## ✓ Non-blocking assignment

- Evaluations and assignments are executed **at the same time without regard to orders or dependence upon each other**
- Syntax : **<variable> <= <expression>;**
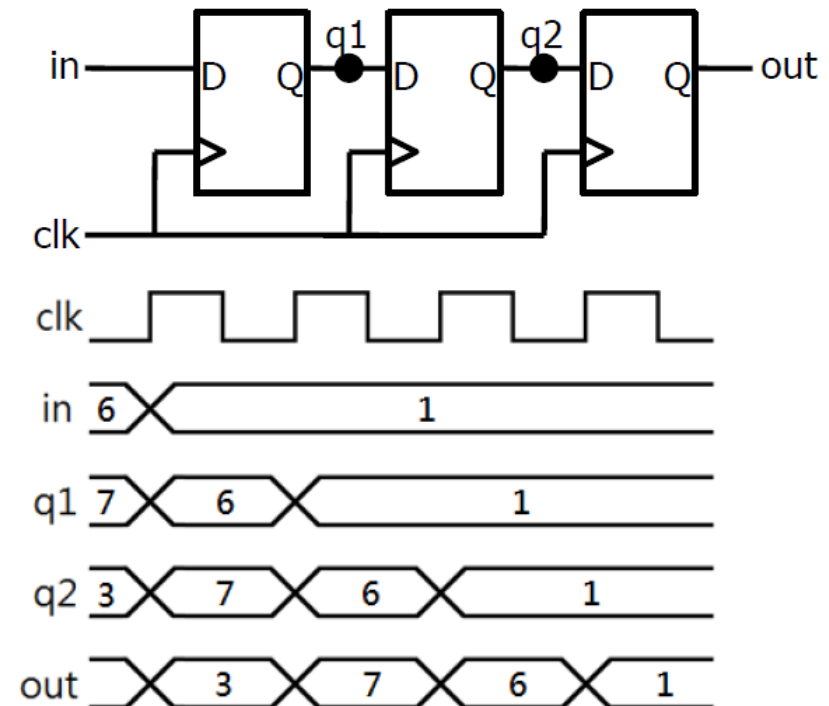
## ✓ Example

```
always @(posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```




# Assignment in Sequential Circuit

## ✓ Blocking assignment

- Evaluations and assignments are **immediate** and **in order**
- Syntax : **<variable> = <expression>;**
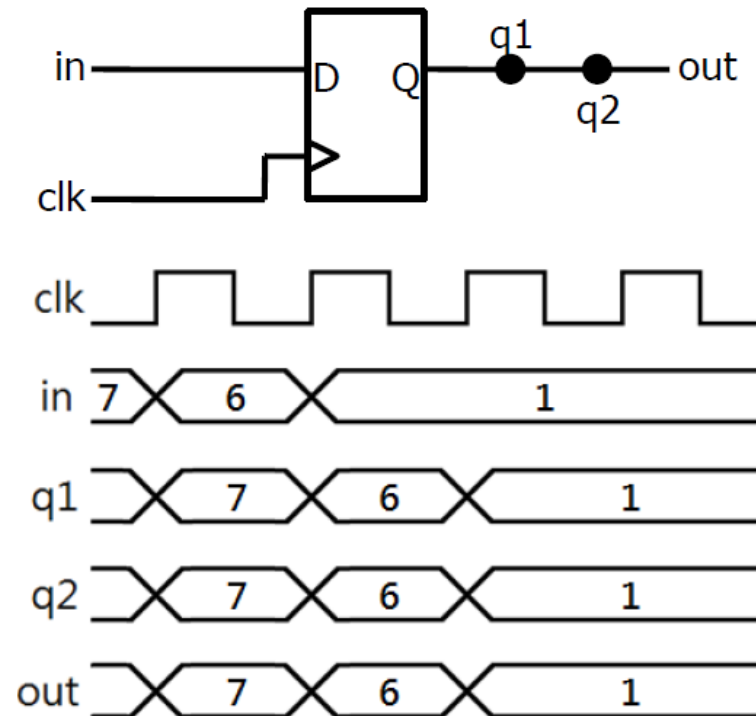
## ✓ Example



```
always @(posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```



# Combinational v.s. Sequential

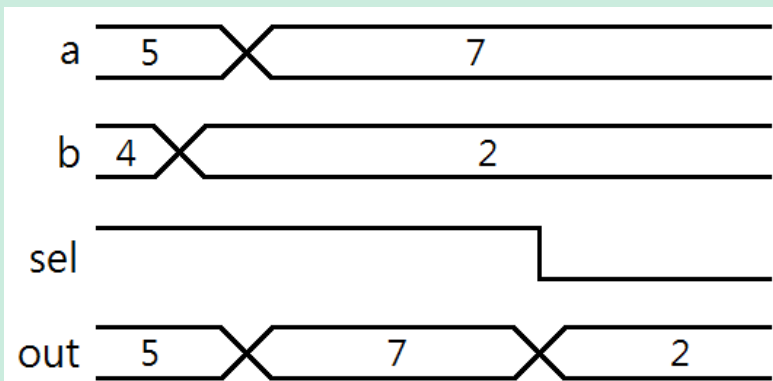
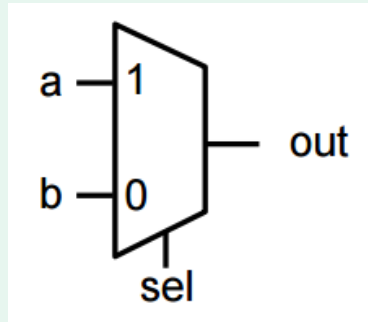
## Combinational

```
always@(*)
begin
    if(sel) out = a;
    else    out = b;
end
```


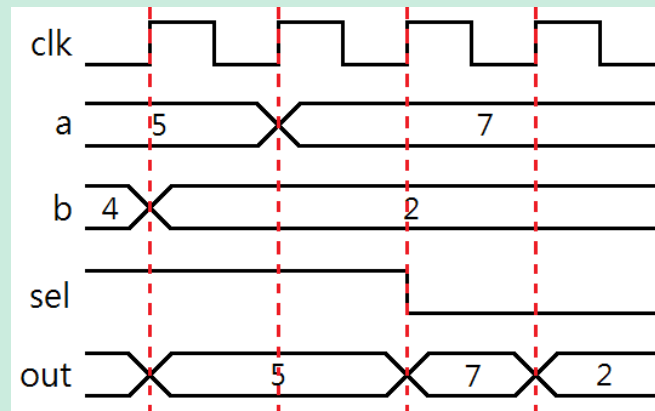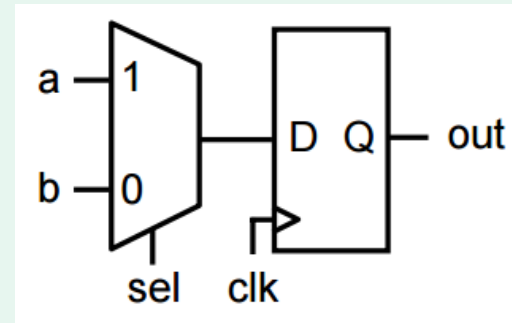
## Sequential


```
always@(posedge clk)
begin
    if(sel) out <= a;
    else    out <= b;
end
```



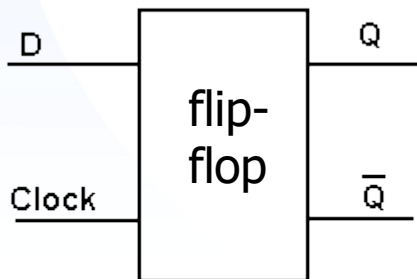
# Sequential Circuit

- ✓ **Sequential block**
  - use **non-blocking** assignments
- ✓ **Combinational block**
  - use **blocking** assignments
- ✓ **Comb./Seq. logic should be separated**

```
always@(posedge clk)
begin
    Q <= D;
end
```


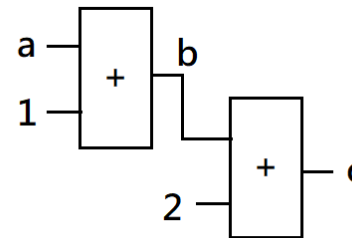
```
always@*
begin
    b = a + 1;
    c = b + 2;
end
```



# Outline

## ✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ **Reset**

✓ Coding Style

✓ Generate & For loop




# Synchronous Reset (1/2)
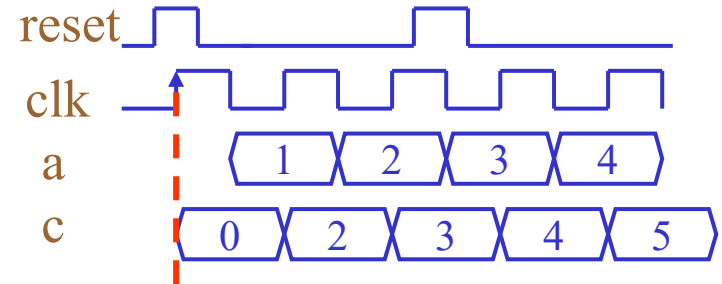
## ✓ Register with synchronous reset

- Syntax: `always@(posedge clk)`

```
always @(posedge clk) begin
    if (reset) c <= 0;
    else c <= a+1;
end
```




## ✓ Advantages

- Glitch filtering from reset combinational logic


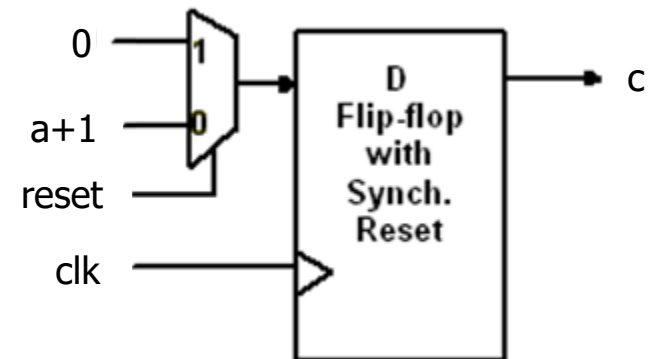
## ✓ Disadvantages

- Can't be reset without clock signal
- May need a pulse stretcher
  - Guarantee a reset pulse wide enough
- Larger area
- Increase critical path



# Synchronous Reset (2/2)

✓ Advantage: glitch filtering

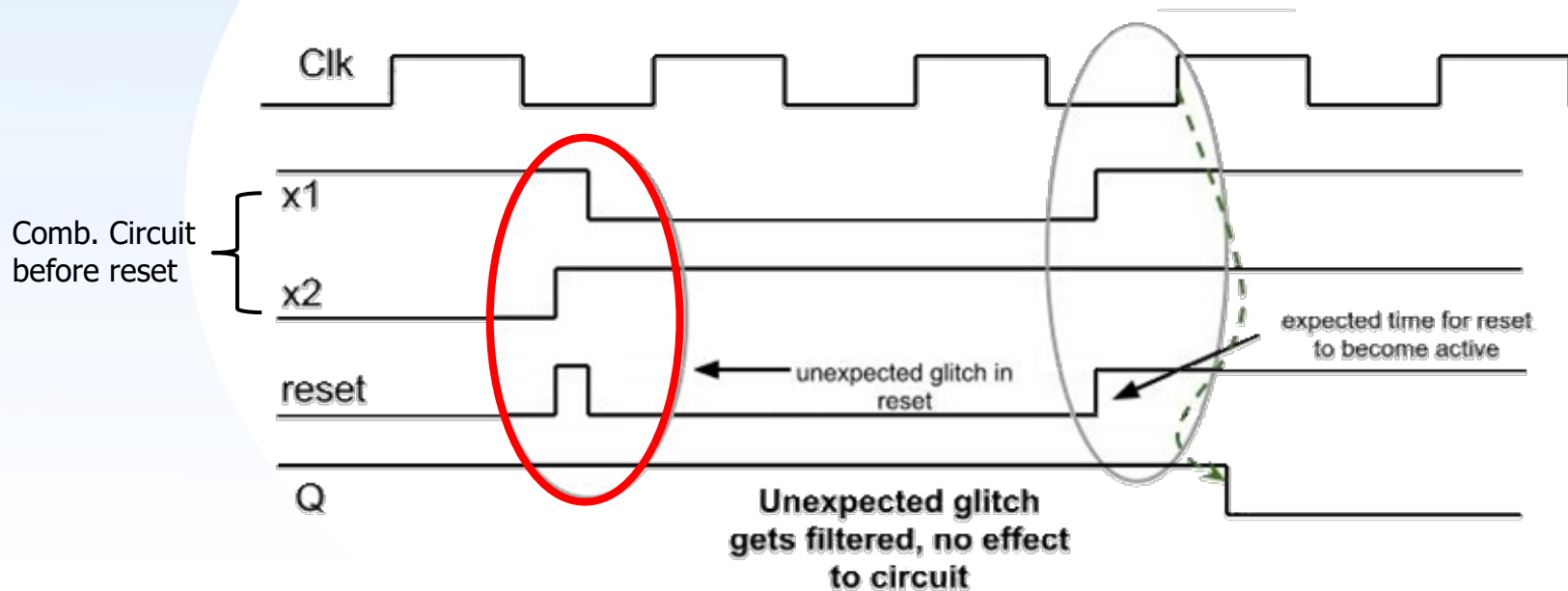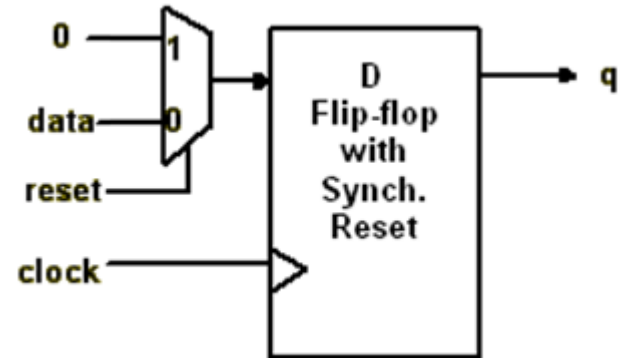




# Asynchronous Reset
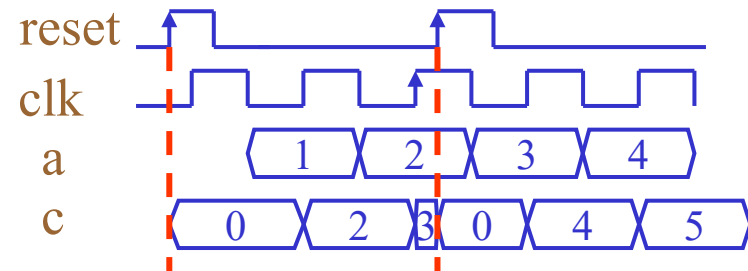
## ✓ Register with asynchronous reset

- Syntax: **always @(posedge clk or negedge reset)**

```
always @(posedge clk or posedge reset)
begin
    if (reset) c <= 0;
    else c <= a+1;
end
```




## ✓ Advantages

- Reset is independent of clock signal
- Reset is immediate
- Less area
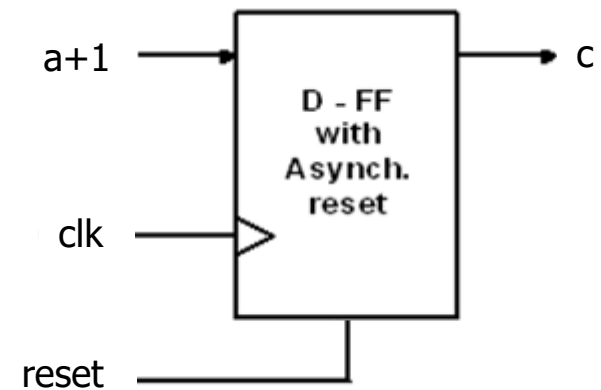
## ✓ Disadvantages


- Noisy reset line could cause unwanted reset
- Metastability


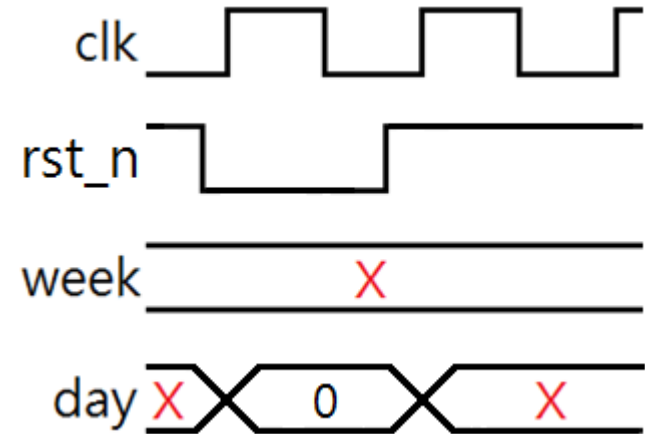
# Avoid Unknown

- ✓ Reset all signals to avoid unknown propagation

**X**always @(posedge clk) begin  
 // if(!rst\_n) week <= 0;  
 week <= week+1;  
end  
always @(posedge clk) begin  
 if(!rst\_n) day <= 0;  
 else day <= week \* 7;  
end



AND	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

OR	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

NOT	output
0	1
1	0
X	X
Z	X



# Outline

## ✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ Reset

✓ Coding Style

✓ Generate & For loop



# Coding Styles (1/2)

✓ **Naming should be readable**

✓ **Synthesizable codes**

- assign, always block, called sub-modules, if-then-else, cases, parameters, operators (+ - \* / and or)

✓ **Data has to be described in one always block**

- Multiple source drive is not valid

**X**

```
always @(posedge clk) begin
    out <= out+1;
end
always @(posedge clk) begin
    out <= a;
end
```

✓ **Only “<=” assignments in sequential blocks**

- And “=” assignments in combinational blocks

**X**

```
always @(posedge clk) begin
    if(reset) out = 0;
    else out <= out+in;
end
```



# Coding Styles (2/2)

- ✓ **Do not put many variables in one `always` block**
  - Except shift registers or registers with similar properties

```
always @(posedge CLK) begin
    q2 <= in;
    if(sel==0) out <= q2;
    else if(sel==1) out <= q3;
    else out <= out;
end
```

**bad**

```
always @(posedge CLK) begin
    q2 <= in;
end
always @(posedge CLK) begin
    if(sel==0) out <= q2;
    else if(sel==1) out <= q3;
    else out <= out;
end
```

**suggested**

- ✓ **Use FSM (Finite State Machine)**



# Outline

## ✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ Reset

✓ Coding Style

✓ **Generate & For loop**



# Generate

## SystemVerilog

3.1a	{	assertions	mailboxes	from C / C++		
		test program blocks	semaphores	classes	dynamic arrays	
		clocking domains	constrained random values	inheritance	associative arrays	
		process control	direct C function calls	strings	references	
3.0	{	interfaces	packages	int	globals	break
		nested hierarchy	2-state modeling	shortint	enum	continue
		unrestricted ports	packed arrays	longint	typedef	return
		automatic port connect	array assignments	byte	structures	do-while
		enhanced literals	queues	shortreal	unions	++ -- += -= *= /=
		time values and units	unique/priority case/if	void	casting	>>= <<= >>>= <<<=
		specialized procedures	compilation unit space	alias	const	&=  = ^= %=

## Verilog-2001

ANSI C style ports	standard file I/O	(* attributes *)	multi dimensional arrays
<b>generate</b>	\$value\$plusargs	configurations	signed types
localparam	`ifndef `elsif `line	memory part selects	automatic
constant functions	@*	variable part select	** (power operator)

## Verilog-1995

modules	\$finish \$fopen \$fclose	initial	wire reg	begin-end	+	=	*	/
parameters	\$display \$write	disable	integer real	while		%		
function/tasks	\$monitor	events	time	for forever	>>	<<		
always @	`define `ifdef `else	wait # @	packed arrays	if-else				
assign	`include `timescale	fork-join	2D memory	repeat				



# For Loop

## ✓ For loop in Verilog

- Duplicate same function
- Very useful for doing reset and iterated operation

```
reg [3:0] temp;  
integer i;  
always @(posedge clk) begin  
  for (i = 0; i < 3 ; i = i + 1) begin: for_name  
    temp[i] <= 1'b0;  
  end  
end
```

=

```
always @(posedge clk) begin  
  temp[0] <= 1'b0;  
  temp[1] <= 1'b0;  
  temp[2] <= 1'b0;  
end
```





# Generate(1/2)

## ✓ How to use for loop with generate?

- For loop in generate : four always blocks
- Regular for loop : one always block

```
reg [3:0] temp;  
genvar i;  
generate  
for (i = 0; i < 4 ; i = i + 1) begin: for_name  
    always @(posedge clk) begin  
        temp[i] <= 1'b0;  
    end  
end  
endgenerate
```

Generate block(suggest)

```
reg [3:0] temp;  
integer i;  
always @(posedge clk) begin  
    for (i = 0; i < 4 ; i = i + 1) begin:  
        temp[i] <= 1'b0;  
    end  
end
```


Regular for loop



# Generate(2/2)

```
reg [3:0] temp;  
  
genvar i;  
generate  
for (i=0 ; i <4; i = i+1)begin loop_1  
    always@(*)begin  
        temp[i] = operand1[i] & operand2[i];  
    end  
end  
endgenerate
```

always block in for loop with  
genvar

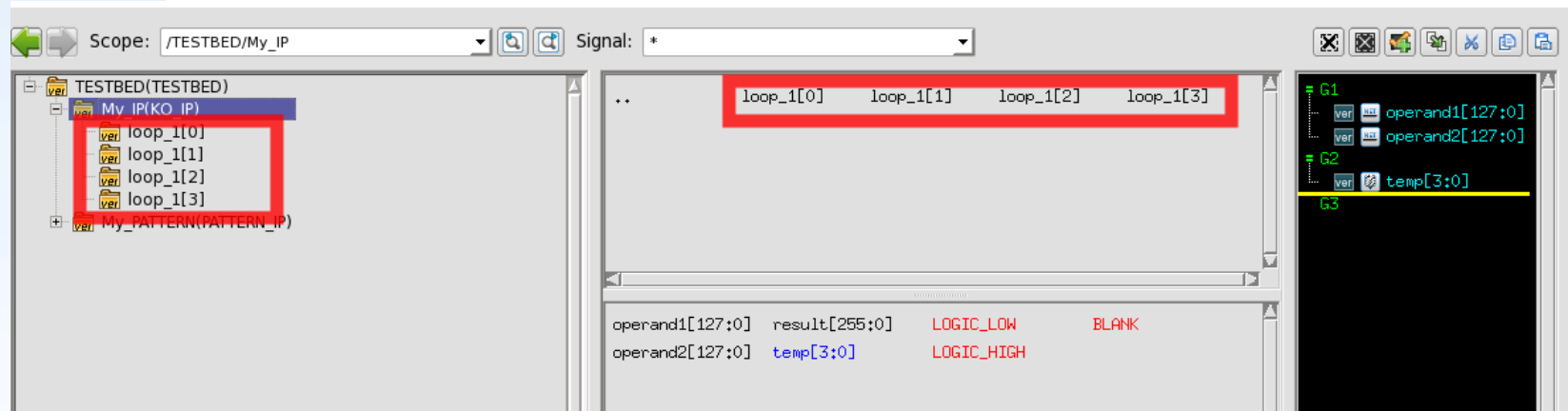

4 always block  
instance

# For Loop/Generate Example

- ✓ **Example**
  - Copy a module for 3 times
- ✓ **Generate:**

```
module A();  
endmodule  
  
module B();  
  genvar i;  
  generate  
    for(i=0; i<3; i=i+1) begin  
      A uA(...)  
    end  
  endgenerate  
endmodule
```



```
module A();  
...  
endmodule  
  
module A();  
...  
endmodule  
  
module A();  
...  
endmodule
```

# For Loop/Generate Example

- ✓ **Example**
  - Copy a module for 3 times
- ✓ **Generate:**

```
module A();  
endmodule  
  
module B();  
for(i=0; i<3; i=i+1) begin  
    A uA(...)  
end  
endmodule
```



# For Loop/Generate Summary

- ✓ **In design -- need to be synthesizable**
  - Use generate
- ✓ **In pattern – don't need to be synthesizable**
  - Use for loop.
- ✓ **Avoid using for loop in your design!!!**



# Outline


- ✓ Section 1 Sequential Circuits
- ✓ **Section 2 Finite State Machine**
- ✓ Section 3 Timing
- ✓ Section 4 Synthesis and Design Compiler



# Finite State Machine

## ✓ Example: Vending machine

Coke \$25  
Pepsi \$25  
Sprite \$25

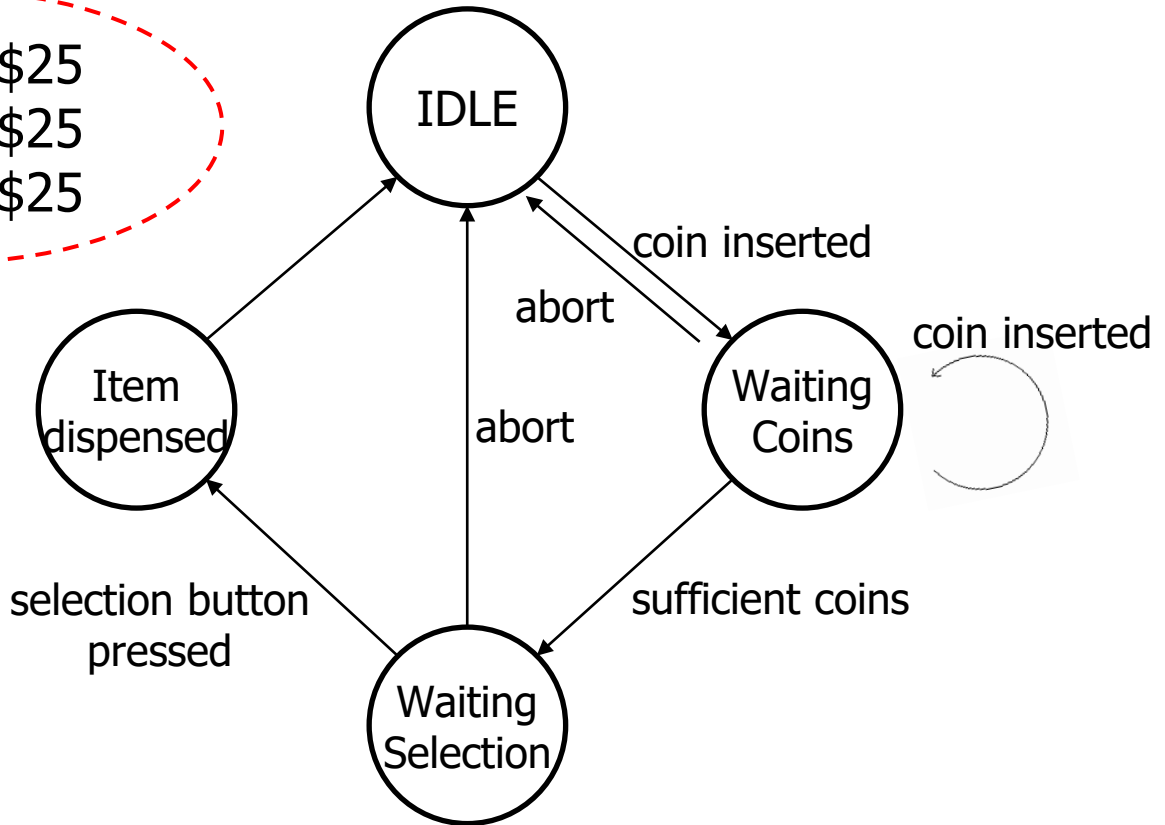


# Finite State Machine

## ✓ Finite state machine

- Powerful model for describing a sequential circuit
- Divide a sequential circuit operation into finite number of states.
- A state machine controller can output results depending on the input signal, control signal and states.
- As different input or control signal changes, the state machine will take a proper state transition.

## ✓ State diagram

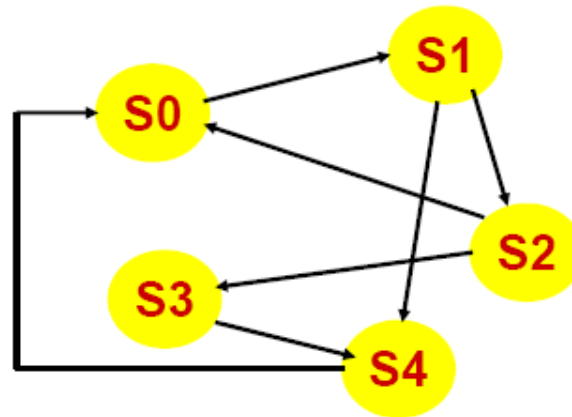



# Mealy and Moore Machines(1/3)

## ✓ Mealy machine



- The outputs depend on the current state and inputs
- If input changes, output also changes

## ✓ Advantages

- Less number of states are required
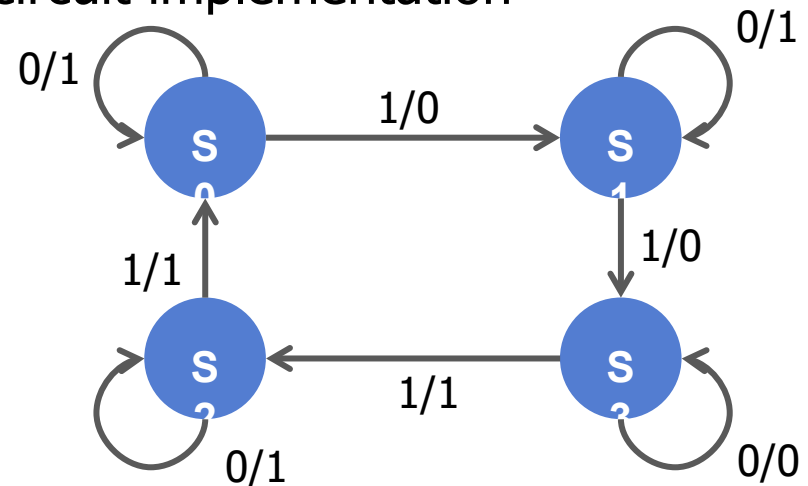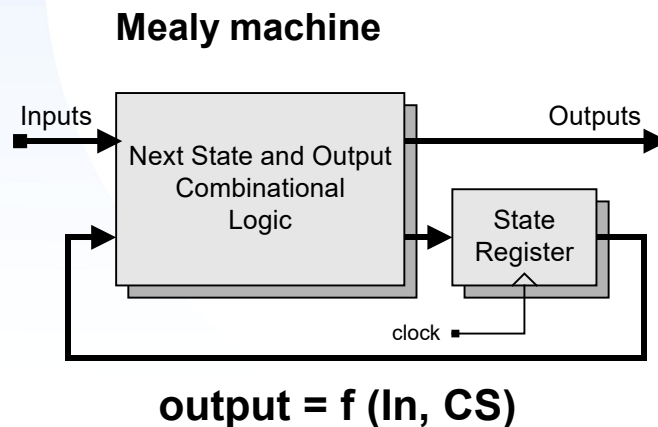
## ✓ Disadvantages

- More hardware requirements for circuit implementation



# Mealy and Moore Machines(2/3)

## ✓ Moore machine

- The outputs depend on the current state only
- Inputs affect outputs but not immediately


## ✓ Advantage

- Safer. Outputs change at clock edge


## ✓ Disadvantage

- More states are required

Moore machine

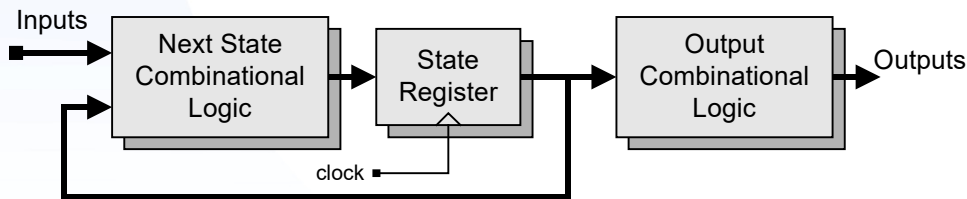

$$\text{output} = f(\text{CS})$$

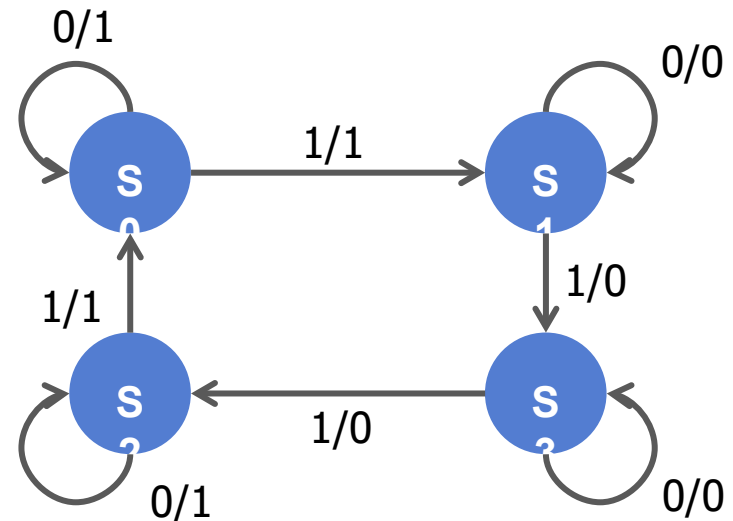

# Mealy and Moore Machines(3/3)

- ✓ FSM coding style
  - Separate CS, NS and OL

Current  
State

```
always @(posedge clk)
    current_state <= next_state;
```

Next  
State

```
always @(current_state or In)
case (current_state)
state_0: case(In)
    In0: next_state = state_value1;
    In1: next_state = state_value2;
    .....
endcase
.....
default : .....
endcase
```

If it is not full case and without **default case**, latch will be incurred!

Mealy  
machine

Moore  
machine

Output  
Logic

```
always @(current_state or In)
    Z = values;
```

```
always @(current_state)
    Z = values;
```



# FSM Coding Style(1/2)

## ✓ Separate current state, next state and output logic

### Current State

```
always @(posedge clk or negedge rst_n) begin
    if (!rst_n) current_state <= IDLE;
    else current_state <= next_state;
end
```

Use parameters for readability

### Next State

```
always @(*) begin
    if(!rst_n) next_state=IDLE;
    else begin
        case(current_state)
            STATE_1: begin
                if (in==in_1) next_state=STATE_2;
                else next_state=current_state;
            end
            STATE_2: .....
            ....
            default: next_state=current_state;
        endcase
    end
end
```

If it's not full case and without default case, latch would be incurred!


### Output Logic

```
always@(posedge clk or negedge rst_n) begin
    if (!rst_n) out <= 0;
    else if (current_state==STATE_3) out <= output_value;
    else out <= out;
end
```



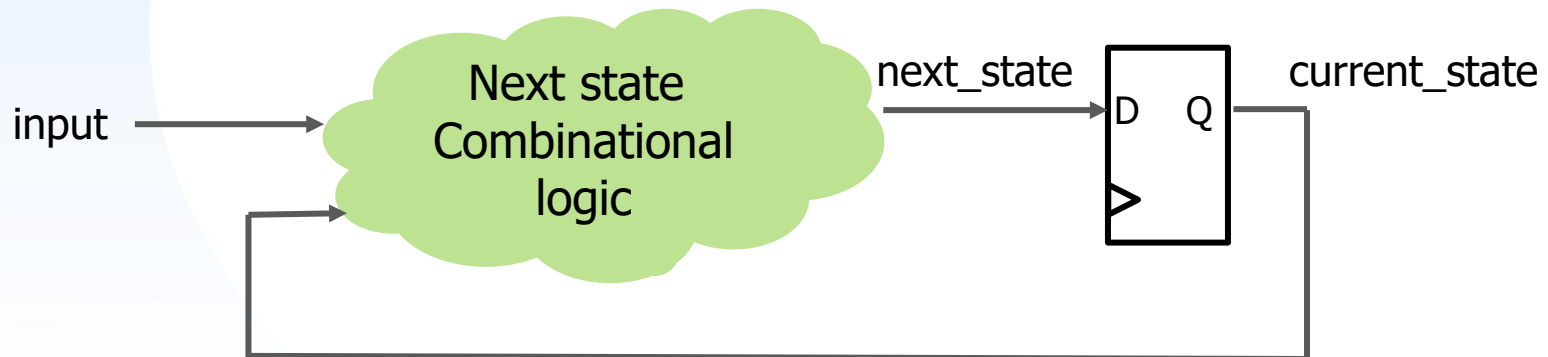
# FSM Coding Style(2/2)

- ✓ **current\_state**
  - Sequential circuit
- ✓ **next\_state**
  - Combinational circuit


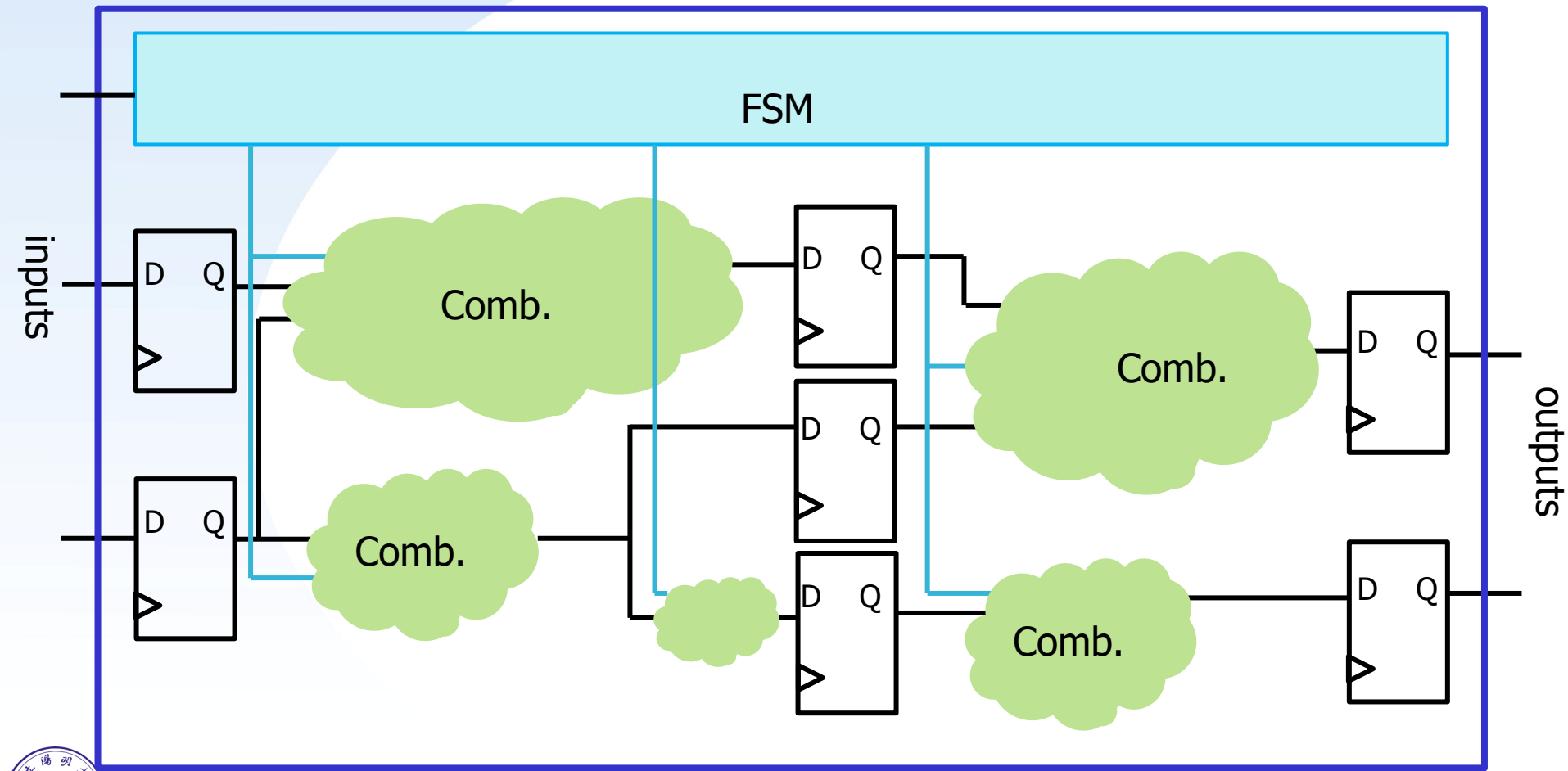
# Why FSM?

- ✓ FSM can be referred to as the controller and status of the whole module



# Outline


- ✓ Section 1 Sequential Circuits
- ✓ Section 2 Finite State Machine
- ✓ **Section 3 Timing**
- ✓ Section 4 Synthesis and Design Compiler



# Timing Check (1/2)

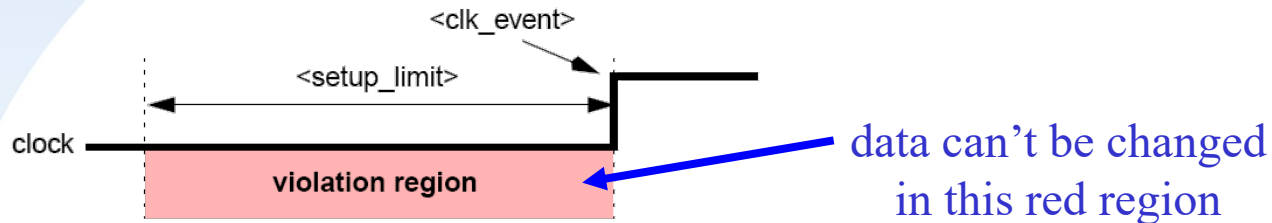
## ✓ Setup time check

- The `$setup` system task determines whether a data signal remains stable for a minimum specified time before a transition in an enabling, such as a clock event.


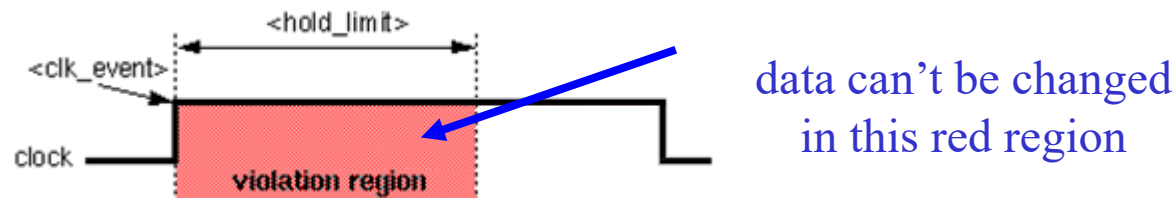
## ✓ Hold time check




- The `$hold` system task determines whether a data signal remains stable for a minimum specified time after a transition in an enabling signal, such as a clock event.





## Timing Check (2/3)

### ✓ Metastability

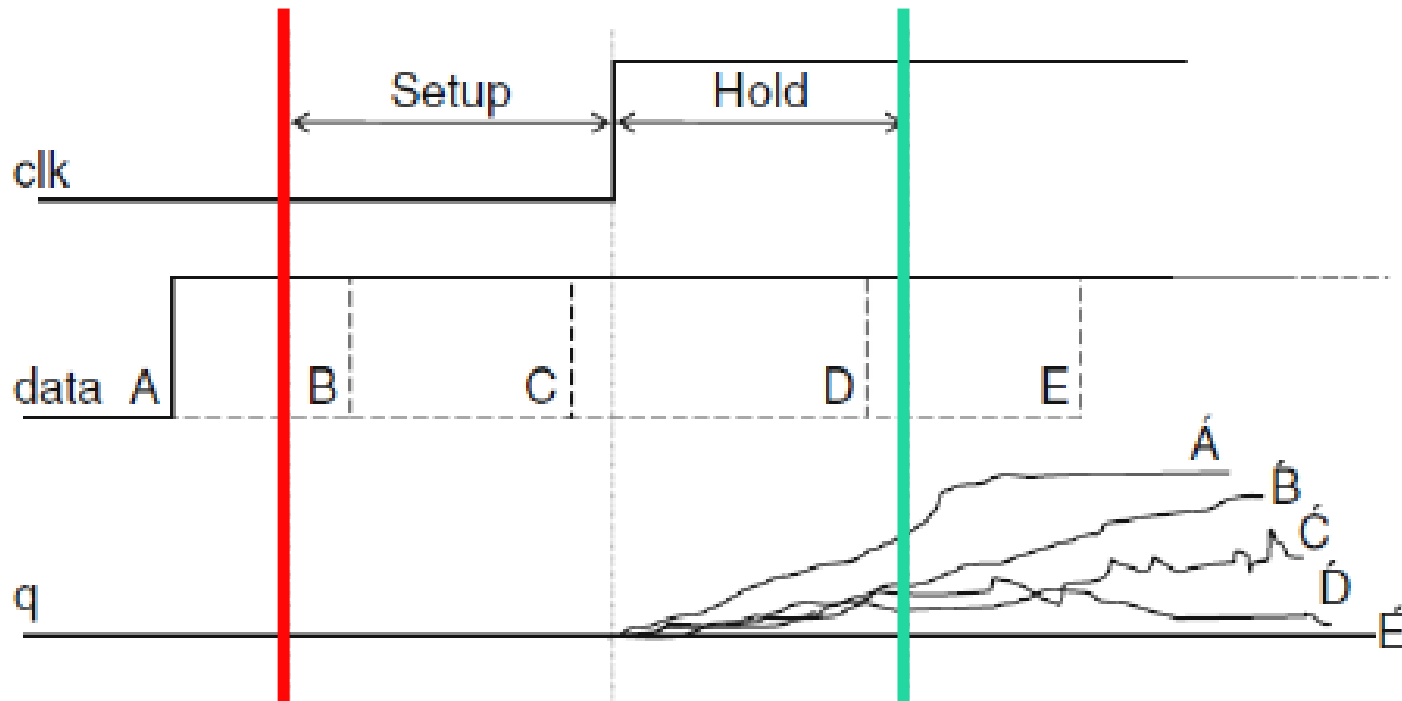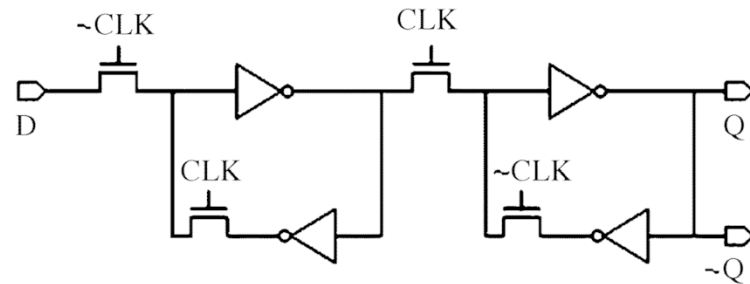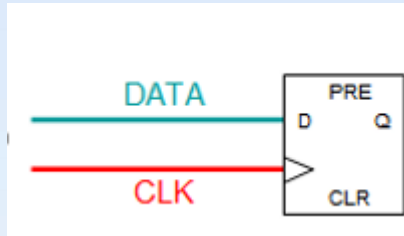

# Timing Check (2/2)

## ✓ Timing report: setup time

clock CLK_1 (rise edge)	2.00	2.00
clock network delay (ideal)	2.00	4.00
clock uncertainty	-0.50	3.50
IN_A_reg[0]/CK (EDFFXL)	0.00	3.50 r
library setup time	-0.42	3.08
data required time		3.08
-----		
data required time		3.08
data arrival time		-3.08
-----		
slack (MET)		0.00

## ✓ Timing report: hold time

Slacks should be **MET!**  
(non-negative)

clock CLK_2 (rise edge)	0.00	0.00
clock network delay (ideal)	4.00	4.00
clock uncertainty	1.00	5.00
IN_B_reg[20]/CK (EDFFXL)	0.00	5.00 r
library hold time	-0.19	4.81
data required time		4.81
-----		
data required time		4.81
data arrival time		-4.82
-----		
slack (MET)		0.01




# Outline

- ✓ Section 1 Sequential Circuits
- ✓ Section 2 Finite State Machine
- ✓ Section 3 Timing
- ✓ **Section 4 Synthesis and Design Compiler**



# Recall: Design Flow

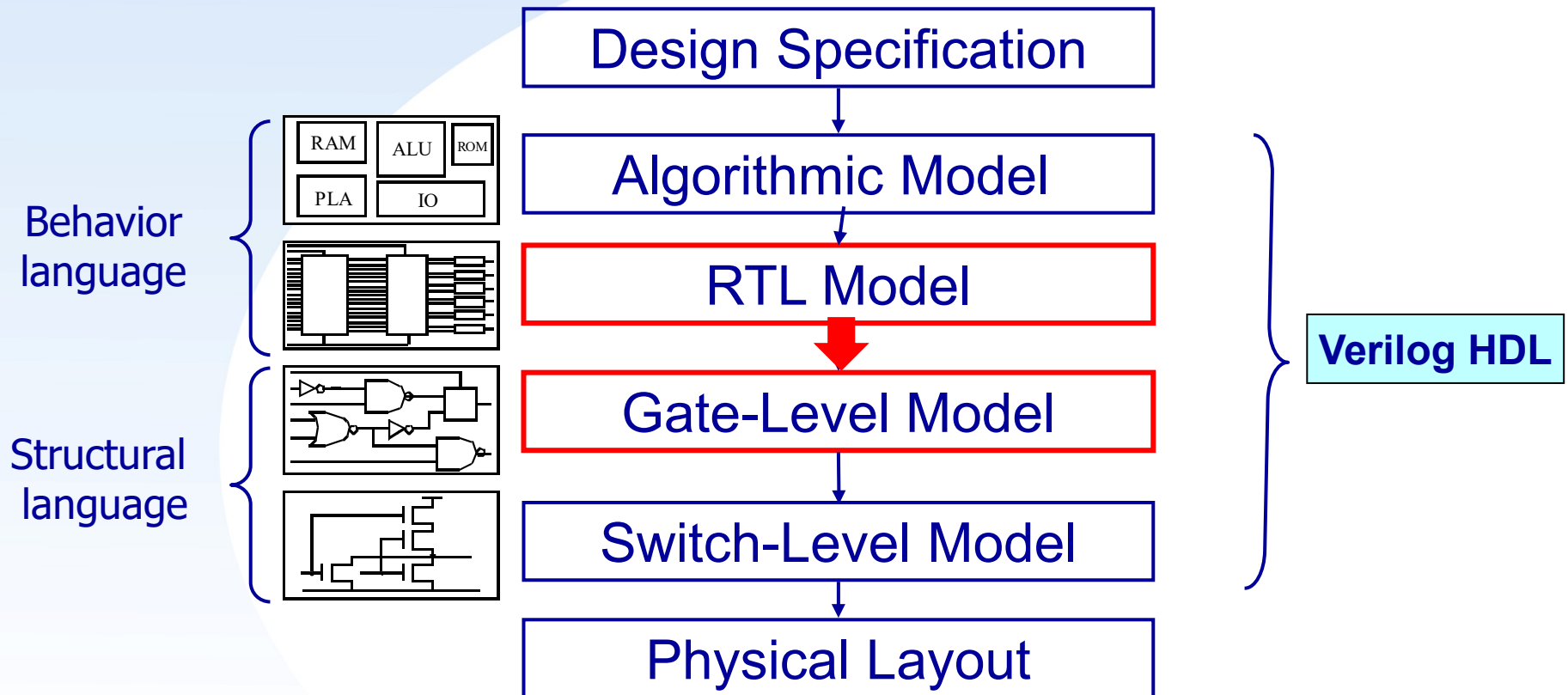

# Logic Synthesis


## ✓ Logic synthesis

- A process by which behavioral model of a circuit is turned into an implementation in terms of logic gates
- Synthesis = **Translation+Optimization+Mapping**



```
assign avg=sum/total;  
always_ff @(posedge clk)  
begin  
    sum=sum+score*weight;  
end
```

**HDL Source**

**Translate**

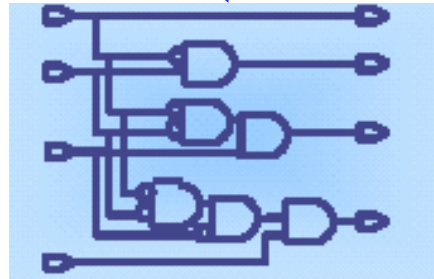

**Optimize + Map**

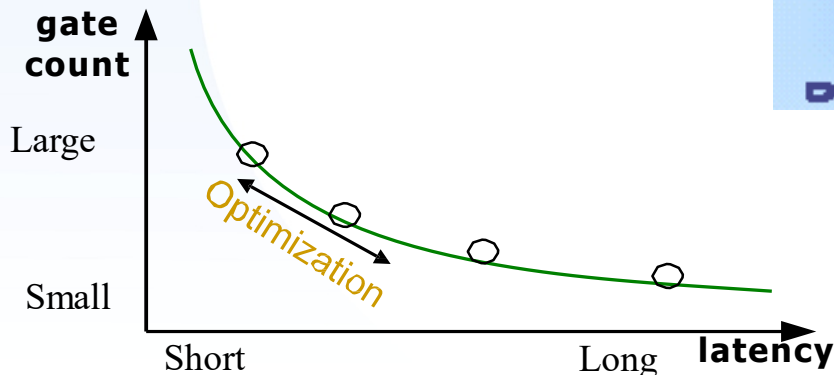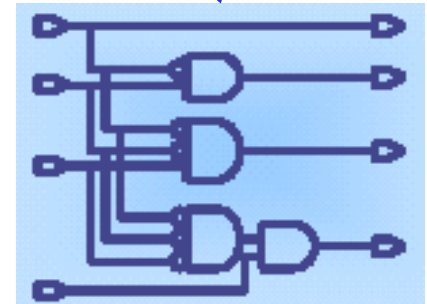

**Target Technology**

# Design Compiler

## ✓ Design compiler

- A tool by Synopsys, Inc. that synthesizes your HDL designs (**Verilog**) into optimized technology-dependent, **gate-level** designs.
- It can optimize both combinational and sequential designs for speed, area, and power.

