NYCU-EE IC LAB - Spring2023

Lab01 Exercise

Design: Chinese Course


Data Preparation

- 1. Extract files from the TA directory:
- % tar xvf ~iclabta01/Lab01.tar
- 2. The extracted LAB directory contains:
 - a. Practice/: example code
 - b. Exercise/: your design

Design Description and Examples

At the end of the Chinese course at National Yang Ming Chiao Tung University, the teacher CC decided to entrust you with adjusting the scores of the seven students taking the course, after the score adjustment, the teacher CC would like to know how many students passed/failed the course and the ranking of the scores.

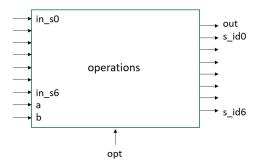You will receive a sequence with 4-bit 7 scores {in_s0, in_s1, in_s2, in_s3, in_s4, in_s5, in_s6}, a 3-bit signal opt, a 2-bit signal a and a 3-bit signal b. Then you should do some operations in the following order to receive the number of passing students and ranking of the scores:



First, please do the 5 possible operations in the following order:

1. Signed/Unsigned	If opt[0] is 1, the 7 numbers will be regarded as 2's complement							
	signed values, which means that there MSB is signed bit.							
	For example, in_n0=4'b1010, then its value is -6.							
	in_n0=4'b0010, then its value is 2							
	If opt[0] is 0 , the 7 numbers will be regarded as unsigned values.							
	For example, in_n0=4'b1010, then its value is 10							
	in_n0=4'b0010, then its value is 2							
2. Sort	If opt[1] is 1, sort the scores from the largest to the smallest.							
	If opt[1] is 0, sort the sequence from the smallest to the largest.							
	And output the corresponding student id (s_id0~s_id6) after sorting.							

For example,	if original	scores are	$\{2, -1, \dots, \dots, -1, \dots, $. 3.	5. 5.	43	}}
I of champic,	, ii original	i scores are	14, 1	, ,,	$\mathcal{I}_{\mathcal{I}}$, –, –	′ (

Corresponding student id : {0, 1, 2, 3, 4, 5, 6}

When opt[1] is 1

Order of scores becomes $\{5, 5, 4, 3, 2, -1, -3\}$.

Corresponding outputs **s id0~s id6**: {3, 4, 5, 2, 0, 1, 6}

When opt[1] is 0

Order of scores becomes {-3, -1, 2, 3, 4, 5, 5}.

Corresponding outputs **s id0~s id6**: {6, 1, 0, 2, 5, 3, 4}

			- 4 0' James				
original score	2	-1	3	5	5	4	-3
original student id s_id	0	1	2	3	4	5	6
Score after Sorting & opt[1]=1	5	5	4	3	2	-1	-3
Corresponding student id s_id	3	4	5	2	0	1	6
Score after Sorting & opt[1]=0	-3	-1	2	3	4	5	5
Corresponding student id s_id	6	1	0	2	5	3	4

Note. If encountering the same score, always output the student id in **ascending order**.

3. Calculate

Calculate the passing score.

- 1. Calculate average $\mu = \frac{\sum_{i=0}^{6} in_{i}S_{i}}{7}$ (round down)
- 2. Calculate passing score= μ a

For example, if original scores are $\{2, -1, 3, 5, 5, 4, -3\}$, a=1

Average $\mu = \frac{[2+(-1)+3+5+5+4+(-3)]}{7} = 2 \text{(round down)}$

Passing score = $\mu - a = 1$

Note. a is an input signal.

4. Linear-	If the student's score is negative , adjust the score to $\frac{score}{a+1} + b$.					
transformation	Otherwise, adjust the score to $(a+1) * score + b$					
	e.g. original scores: $\{2, -1, 3, 5, 5, 4, -3\}$ and parameter $a = 1, b = 3$					
	1st number of new scores: $2 * 2 + 3 = 7$					
	2nd number of new scores: $(-1)/2$ (round down) $+3=0+3=3$					
	3rd number of new scores: $3 * 2 + 3 = 9$					
	4th number of new scores: $5 * 2 + 3 = 13$					
	5th number of new scores: $5 * 2 + 3 = 13$					
\	6th number of new scores: $4 * 2 + 3 = 11$					
	7th number of new scores: $-3/2$ (round down) $+3=-1+3=2$					
	After linear transformation, new scores: {7, 3, 9, 13, 13, 11, 2}					
	Note. You should round-down first if $\frac{score}{a+1}$ is not integer.					
5. Count	If opt[2] is 1, count the number of students who failed.					
	If opt[2] is 0, count the number of students who passed.					
	If one's score is smaller than the passing score, this student failed.					
	Otherwise, this student passed.					
	e.g. original scores: $\{2, -1, 3, 5, 5, 4, -3\}$ and parameter $a = 1, b = 3$					
	After linear transformation, new scores: {7, 3, 9, 13, 13, 11, 2} and					
	Passing score=1.					
	Thus, if opt[2] = 1, output $\underline{\mathbf{out}}$ equals to 0 .					
	If opt[2] = 0, output <u>out</u> equals to 7.					

The summary of the description and specifications are as followings:

Input	Bit	Description
Signal	Width	
in_s0	4	The score of the first student.
		If opt[0] is 0, in_s0 will be regarded as unsigned integer
		and ranged from 0~15.
		If opt[0] is 1, in_s0 will be regarded as 2's complement
		signed integer and ranged from -8~7 .
in_s1	4	The score of the second student.
		If opt[0] is 0, in_s1 will be regarded as unsigned integer

	-		11 C 0 15
		<u>yste</u>	and ranged from 0~15.
		0:1:	If opt[0] is 1, in_s1 will be regarded as 2's complement
		$\mathcal{O}III$	signed integer and ranged from -8~7.
in_s2 4			The score of the third student.
			If opt[0] is 0, in_s2 will be regarded as unsigned integer
		A	and ranged from 0~15.
		Multim	If opt[0] is 1, in_s2 will be regarded as 2's complement
			signed integer and ranged from -8~7.
in_s3		4	The score of the fourth student.
		$\langle $	If opt[0] is 0, in_s3 will be regarded as unsigned integer
			and ranged from 0~15.
		Y	If opt[0] is 1, in_s3 will be regarded as 2's complement
			signed integer and ranged from -8~7.
in_s4		4	The score of the fifth student.
			If opt[0] is 0, in_s4 will be regarded as unsigned integer
			and ranged from 0~15.
			If opt[0] is 1, in_s4 will be regarded as 2's complement
			signed integer and ranged from -8~7.
in_s5		4	The score of the sixth student.
			If opt[0] is 0, in_s5 will be regarded as unsigned integer
			and ranged from 0~15.
			If opt[0] is 1, in_s5 will be regarded as 2's complement
			signed integer and ranged from -8~7.
in_s6		4	The score of the seventh student.
			If opt[0] is 0, in_s6 will be regarded as unsigned integer
			and ranged from 0~15.
			If opt[0] is 1, in_s6 will be regarded as 2's complement
			signed integer and ranged from -8~7.
opt		3	Operator for different mode. The operation will be
			encode as following:
			opt[0]: 1: Signed. 0: Unsigned
			opt[1]: 1: Sort from L->S. 0: Sort from S->L.
			opt[2]: 1: fail 0: pass
a		2	Parameter of linear transformation.

	Syste	Ranged from 0~3.
b		Parameter of linear transformation. Ranged from 0~7.
		Implementation

Output	Bit	Wireless Description
Signal	Width	dia
out	3	If opt[2] is 0, output the number of people who passed.
		If opt[2] is 1, output the number of people who failed.
	/ // :	Ranged from 0~7.
s_id0	3	The student id corresponds to the first score after sorting.
	1	Ranged from 0~7.
s_id1	3	The student id corresponds to the second score after
		sorting.
		Ranged from 0~7.
s_id2	3	The student id corresponds to the third score after
		sorting.
		Ranged from 0~7.
s_id3	3	The student id corresponds to the fourth score after
		sorting.
		Ranged from 0~7.
s_id4	3	The student id corresponds to the fifth score after
		sorting.
		Ranged from 0~7.
s_id5	3	The student id corresponds to the sixth score after
		sorting.
		Ranged from 0~7.
s_id6	3	The student id corresponds to the seventh score after
		sorting.
		Ranged from 0~7.

Inputs& Outputs


- 1. The input signals: in_s0, in_s1, in_s2, in_s3, in_s4, in_s5 and in_s6 are 4-bit inputs.
- 2. The input signal **opt** is a 3-bit input indicated whether to do the operations and which equation to use to get the final result and the input signal **a** and **b** are the parameters of linear transformation.

- 3. The output **out** is an unsigned number ranged from **0~7**. This represents the number of students passed/failed.
- 4. The output signals : **s_id0**, **s_id1**, **s_id2**, **s_id3**, **s_id4**, **s_id5**, **s_id6** are 3-bit outputs which represent the student ids.

Specifications

- 1. Top module name : CC (File name: CC.v)
- 2. Input pins : in_s0, in_s1, in_s2, in_s3, in_s4, in_s5, in_s6, opt, a, b
- 3. Output pins : out, s id0, s id1, s id2, s id3, s id4, s id5, s id6

Block Diagram

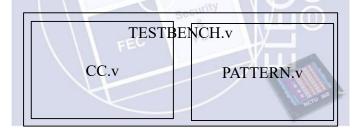

Grading Policy

The performance is determined by the area of your design. The less area your design has, the higher grade you get. Try to reach better performance by thinking your architecture before coding.

Function Validity: 70% Performance: area 30%

Note

- 1. Submit your design (CC.v) at Lab01/Exercise/09 SUBMIT
- 2. Submit your design through Lab01/Exercise/09 SUBMIT/01 submit
 - a. 1st demo deadline: 2023/02/27(Mon.) 12:00:00
 - b. 2nd demo deadline: 2023/03/01(Wed.) 12:00:00
- 3. If your file violates the naming rule, you will lose 5 points.
- 4. Don't use any wire/reg/submodule/parameter name called *error*, *congratulations*, *latch* or *fail* otherwise you will fail the lab. Note: * means any char in front of or behind the word, e.g: error note is forbidden.

Be careful about all details!

Template folders and reference commands:

In RTL simulation, the name of template folder and reference commands is:

1. 01_RTL (RTL simulation):

./01 run

2. 02 SYN/ (Synthesis):

./01 run dc

(Check latch by searching the keyword "Latch" in 02_SYN/syn.log)

(Check the design's timing in /Report/ CC.timing)

(Check the design's area in /Report/ CC.area)

3. 03 GATE/ (Gate-level simulation):

./01 run

4. 09 SUBMIT/ (submit your files):

./01_submit ./02_check

You can key in ./09 clean up to clear all log files and dump files in each folder

System Integration Example Waveform Input and output signal: 111CO11 Implementation

			The second second second				
□ opt[2:0]	7	(6	0	(6	3	1	0
· 🔤 jn_s0[3:0]	0	d	5	9	0	6	2
lor 🛃 in_s1[3:0]	6	(f	4	1) 8) d	е
ler 🜓 in_s2[3:0]		8	9	3	(f	b	3
· 🖟 🖢 in_s3[3:0]	5	(b	6	4	7)	3
in_s4[3:0] in_s4[3:0]	0	5	6	3	8	6	f
ler 🚽 in_s5[3:0]	8	C	a	γ ο	3	7	f
· 🛅 in_s6[3:0]	9	8	0	(f	, •	7	5
· lor → a[1:0]		3	1	O	1	2	1
lor 🚽 b[2:0]	1	4	5	6	7	5	7
- Mar D- s_id0[2:0]		1		6	3	2	0
S_id1[2:0]	3	(0	1	O	5	1	2
Ior D s_id2[2:0]	0	(5	0	3	, 0)	3
ler ▶ s_id3[2:0]	4)		2	(6) o	6
- Mm D- s_id4[2:0]	6	2		4	2	4	1
. Dr D- s_id5[2:0]	2	(6	2	X	1	5	4
lor ▶ s_id6[2:0]	5	4		5	4	6	5
In b out[2:0]		0	7	Y 0	ĭ		7